

How a Fuse Works Worksheet

Observations

Draw the completed circuit as it was initially set up by your instructor. Label the following: battery, lightbulb, fuse.

Discussion Questions

1. How was a short circuit created? Why is it called a short circuit?
2. Describe what happened after the short circuit was created. What is the purpose of the fuse?
3. Ohm's law describes the relationships between current (I), voltage (V), and resistance (R) and is represented by the equation $V = I \times R$. The lightbulb provides a certain amount of resistance in the circuit. What effect does creating a short circuit have on the current? Explain in terms of Ohm's law.
4. When a fuse blew in a household circuit, a once-common practice to temporarily reestablish current was to place a penny in place of the melted filament until a new fuse could be obtained. Why is this procedure unsafe?