

## AP Physics 1 Review Questions

### *Integrating Content, Inquiry and Reasoning*

- The resistance through one branch of a circuit is measured to be  $15.0\ \Omega$ . A resistor is added the branch. The resistance is now measured to be  $4.50\ \Omega$ .
  - Was the new resistor added in series or parallel to the branch? Explain how you made your determination.
  - What is the resistance value of the added resistor?
- A circuit is constructed with a  $12.0\text{-V}$  battery and three resistors,  $R_1$ ,  $R_2$ , and  $R_3$ . The resistors are connected in series. The resistance values of  $R_1$  and  $R_2$  are the same. The current entering  $R_3$  is  $158\ \text{mA}$ , and  $R_3$  has a resistance of  $50.0\ \Omega$ .
  - Calculate the resistance of  $R_1$  and  $R_2$ .
  - Calculate the change in potential across the three resistors individually.
- The circuit below is constructed using a voltage source of  $110\ \text{V}$  and five resistors of equal resistance,  $R$ . The current entering  $R_1$  is  $2.01\ \text{A}$ .
  - Determine the value of  $R$ .
  - Calculate the change in potential ( $\Delta V$ ) across  $R_1$ .

